

## Motivation

The motivation behind creating this Arduino-Based Digital Multimeter is multifaceted, stemming from a strong desire for both theoretical understanding and practical application. Primarily, this project serves an educational purpose, providing a deeper understanding of fundamental electronics principles. This includes concepts crucial to circuit analysis and measurement, such as voltage division, Ohm's Law, current sensing, and the methods for continuity testing.

Beyond theoretical learning, the project offers a valuable opportunity for the practical application of microcontrollers. It provides a hands-on environment to learn how to interface various sensors and components directly with an Arduino. Practicing the essential skills of reading analog values from sensors, processing that raw data within the microcontroller, and then displaying the processed information in a clear and user-friendly manner. Moreover, the project is driven by the goal of creating a cost-effective learning tool. By utilizing commonly available and relatively inexpensive components, it's possible to build a functional measuring device that offers an actual, hands-on alternative to purchasing a common multimeter, particularly for mastering basic measurement tasks.


Finally, this effort is fueled by the possibility of customization and exploration. The intention is to develop a versatile platform that is not static but can be potentially expanded or modified in the future. This opens up possibilities for integrating other measurement tasks or adding new features.

## Functionality

This Arduino-based digital multimeter can perform the following measurements and functions:

1. **Voltage Measurement:** Measures DC voltage.
2. **Resistance Measurement:** Measures the resistance of a component.
3. **Continuity Test:** Checks for electrical continuity between two points, providing an audible beep if continuity is detected.
4. **Current Measurement:** Measures DC current (likely up to a few amps, depending on the sensor used).
5. **Mode Selection:** Allows the user to cycle through the different measurement modes using a single push button.
6. **Display:** Shows the selected mode and the measured value on a 16x2 LCD display.

## Appearance

 

## Materials Used:

### 1. Arduino Board (e.g., Uno/Nano):

**Character:** Microcontroller board.

**Role:** The brain of the project. It reads data from analog inputs, processes this data according to the selected mode, controls the LCD display, and activates the speaker.

### 2. LiquidCrystal\_I2C (16x2 LCD):

**Character:** Alpha-numeric display module with an I2C interface.

**Role:** Provides visual feedback to the user, displaying the current measurement mode, measured values, and units. The I2C interface simplifies wiring.

### 3. Voltage Divider (for VOLT\_PIN = A0) [330 $\Omega$ & 220 $\Omega$ Resistor]:

**Character:** A circuit typically made of two resistors ( $R1V = 330.0\ \Omega$ ,  $R2V = 220.0\ \Omega$ ).

**Role:** Scales down the input voltage to a range (0-5V DC) that the Arduino's analog input can safely read. The Arduino measures the voltage across  $R2V$  and calculates the original input voltage.

### 4. Voltage Divider (for RES\_PIN = A1) [10k $\Omega$ Resistor]:

**Character:** A circuit formed by a known reference resistor ( $R_{ref} = 10000.0\ \Omega$ ) and the unknown resistor to be measured.

**Role:** The Arduino measures the voltage at the junction between  $R_{ref}$  and the unknown resistor. Using the known  $V_{ref}$  (5V) and  $R_{ref}$ , it calculates the value of the unknown resistance.

**5. Continuity Test Circuit (for CONT\_PIN = A2) [Optional Resistor]:**

**Character:** A simple circuit where the probes complete a path. The Arduino reads an analog voltage that changes based on whether the path is open or closed (low resistance).

**Role:** Detects if there is a low-resistance path between the test probes. The Arduino reads the analog value and compares it to a threshold (Cont\_thres).

**6. ACS712 Current Sensor (assumed for AMMETER\_PIN = A3):**

**Character:** Hall effect-based linear current sensor. It outputs an analog voltage proportional to the current flowing through it. It has a quiescent (zero current) output voltage (around 2.5V for bidirectional sensors, acs712\_off).

**Role:** Measures the current flowing through a circuit. The Arduino reads the analog voltage output by the sensor, subtracts the offset, and divides by the sensitivity (acs712\_sens) to determine the current.

**7. Push Button (BUTTON\_PIN = 3):**

**Character:** A momentary switch.

**Role:** User interface element. Pressing the button signals the Arduino to change the measurement mode (Voltage, Resistance, Continuity, Current). It's configured with an internal pull-up resistor.

**8. Piezo Speaker (SPEAKER\_PIN = 4):**

**Character:** An electroacoustic transducer that produces sound.

**Role:** Provides audible feedback during the continuity test. It emits a tone when continuity is detected.

## Code Explanation

**1. Relevant Declarations:**

VOLT\_PIN = A0; RES\_PIN = A1; CONT\_PIN = A2; AMMETER\_PIN = A3;  
BUTTON\_PIN = 3; SPEAKER\_PIN = 4; BACKLIGHT\_PIN = 13; R1V = 330.0; R2V  
= 220.0; Vref = 5.0; Rref = 10000.0; Cont\_thres = 1010; acs712\_sens = 0.185;  
acs712\_off = 2.5; Iref = 5.0; LiquidCrystal\_I2C lcd(0x27, 16, 2);

**2. Initialization (setup()):**

Serial communication is started for debugging (Serial.begin(9600)).

Pin modes are set: BUTTON\_PIN as **INPUT\_PULLUP**, SPEAKER\_PIN and  
BACKLIGHT\_PIN as **OUTPUT**.

Speaker is initially off (noTone), backlight is on (digitalWrite(BACKLIGHT\_PIN,  
HIGH)). LCD is initialized (lcd.begin(), lcd.init(), lcd.backlight()), cleared, and a startup  
message is displayed.

**3. Main Loop (loop()):**

updateMode(): Checks the button state to change currentMode.

Mode Change Handling: If currentMode changes, the LCD is cleared, and the speaker is

turned off.

switch (currentMode): Calls the appropriate function based on the currentMode:

- a. case 0: displayMenu(): Shows the menu options on the LCD.
- b. case 1: measureVoltage(): Calls the voltage measurement function.
- c. case 2: measureResistance(): Calls the resistance measurement function.
- d. case 3: checkContinuity(): Calls the continuity test function.
- e. case 4: measureCurrent(): Calls the current measurement function.

A small delay(150) "ms" is used to control the refresh rate.

#### 4. Mode Switching (updateMode()):

Reads the **BUTTON\_PIN** state.

Implements debouncing using **millis()** and a **50ms** debounce delay. If a debounced button press (**LOW state**) is detected, currentMode is **incremented** and wraps around using the modulo operator (% 5) making a **loop**.

#### 5. Voltage Measurement (measureVoltage()):

Reads the analog value from **VOLT\_PIN** (analogRead(VOLT\_PIN)).

Converts ADC value to voltage ( $\text{adc\_voltage} = (\text{adc\_value} / 1023.0) * \text{Vref}$ ). **Note: 1023.0 should be used for float division.**

Calculates the actual input voltage using the voltage divider formula:  $\text{in\_voltage} = \text{adc\_voltage} * (\text{R1V} + \text{R2V}) / \text{R2V}$ .

A small threshold sets in\_voltage to 0.0 if it's very low, likely to avoid noisy near-zero readings.

Displays "Voltage" and the **in\_voltage** value (with " V") on the LCD.

#### 6. Resistance Measurement (measureResistance()):

Reads the analog value from **RES\_PIN** (analogRead(RES\_PIN)).

Calculates Vout (voltage across the unknown resistor).

Handles edge cases:

- a. If sensorValue is **very low** (short circuit or very low R), R is 0.0.
- b. If sensorValue is **very high** (open circuit or very high R), R is -1.0 (representing "OL" - Over Limit).
- c. Calculates resistance R using the voltage divider formula:  $R = \text{Rref} * (1.0 / ((\text{Vref} / \text{Vout}) - 1.0))$ .

Displays "Resistance:" on the LCD as well as the value from **R**

Formats the output: "OL", or value in Ohms, kOhms, or MOhms according to the value.

#### 7. Continuity Check (checkContinuity()):

Reads **CONT\_PIN** 5 times with small delays and averages the value to reduce noise.

Compare the sensorValue to Cont\_thres. If **sensorValue > Cont\_thres** (indicating a closed circuit/low resistance path), it plays a tone on **SPEAKER\_PIN** and displays "**Connected**" on LCD. Otherwise, it stops the tone and displays "**Open**" on the LCD.

#### 8. Current Measurement (measureCurrent()):

Reads **AMMETER\_PIN** 20 times and **averages** the ADC value (adc\_average) to

**smooth** out readings from the ACS712 sensor.  $\text{adc\_average} = \text{adc\_average} > 516.20 ?$

**adc\_average : 511.5;** attempts to adjust the baseline ADC reading. This might be a crude way to handle sensor offset or noise near the zero-current point. 511.5 would be the corresponding that would display 0 current according to calculation later (for 2.5V offset on a 5V Vref system). Converts average ADC value to voltage at the pin: **voltage\_at\_pin = (adc\_average \* 5.0) / 1023.0.**

Calculates current using the ACS712 formula: **I = (voltage\_at\_pin - acs712\_off) / (acs712\_sens).**

Displays "Current:" on the LCD as well as the value I  
Formats the output in mA or A with appropriate spacing.

## Q&A

**Problem: Achieving accurate and stable readings, especially for current measurement with the ACS712 sensor and resistance measurement.**

### ACS712 Noise and Offset Drift:

The ACS712 sensor is susceptible to noise, and its quiescent (zero-current) output voltage can drift slightly with temperature or VCC variations. This makes precise measurement of small currents challenging.

**Resistance Measurement Range and Precision:** Measuring a wide range of resistances accurately with a simple voltage divider can be tricky. Very low or very high resistances push the Vout to the extremes of the ADC range, leading to loss of precision. The code tries to handle "OL" (Over Limit) for very high resistances.

### How it was (or could be) Solved:

**Averaging/Smoothing:** The code already implements averaging for current and continuity readings (for loops summing multiple analogRead() values). This is a good first step to reduce random noise.

### Calibration:

**For ACS712:** The approach would be to first ensure no current is flowing through the sensor. Then temporarily modify the code to continuously read the raw analog value from AMMETER\_PIN and display these readings on the Serial Monitor. By observing a series of these values, identify the most frequently occurring ADC reading, which represents the sensor's actual output at zero current. The most frequent value would then be used to replace the threshold in the line **adc\_average = adc\_average > "CHANGE HERE" ? adc\_average : 511.5.**

### Future Hardware Modifications:

Adding bypass capacitors (e.g., 0.1uF ceramic) close to the VCC pins of the Arduino and sensors (especially ACS712) can help filter power supply noise. Using shielded wires for analog signals in noisy environments, though less common for breadboard projects.

Change the current ordinary resistors to more high-precision resistors to ensure more accurate readings.

### Digital Diagram:

